

# How to Detect Insulation Failures in Electrical Equipment – Part 1

---



Sanjay Pithadia

Insulation deterioration is one of the primary causes of electrical-equipment failure in motors, high-voltage transformers and generators. Insulation failure can cause dangerous voltages, fires, high-fault currents and explosions, damage to equipment and property, personal injury, and fatal accidents. The main causes of insulation failure are dielectric contamination, temperature cycling, excessive overloads, excessive voltage stress due to overvoltage, and aging.

Let's look at two different examples of insulation failures. [Figure 1](#) shows a defective stator winding of a welding alternator and burnt coils at the connection side of the winding. [Figure 2](#) shows a transformer that suffered catastrophic failure due to damaged insulating paper, caused by a lack of timely preventive maintenance.



Figure 1. Defective Stator Winding of a Welding Alternator (Image Source: [WindingPhotos](#))



Figure 2. Catastrophic Failure of a Transformer (Image Source: [OilRegeneration.com](#))

Insulation tests can identify deterioration of insulation before any failure occurs.


The Institute of Electrical and Electronics Engineers (IEEE) Recommended Practice for Testing Insulation Resistance of Rotating Machinery (IEEE 43-2000) describes a procedure for measuring insulation resistance, including typical insulation-resistance characteristics of rotating machinery windings and how these characteristics indicate the winding condition. The standard recommends the minimum acceptable values of insulation resistance for alternating current (AC) and direct current (DC) rotating machine windings. According to IEEE 43-2000, the typical insulation resistance indicating an acceptable condition is 100MΩ and above. Using this measurement as a base, the IEEE standard sets the ranges listed in Table 1.

INSULATION RESISTANCE	JUDGEMENT
100 MΩ or higher	Acceptable.
10 to 100 MΩ	The winding has begun deteriorating. There is no problem with the performance at present. Be sure to perform a periodic inspection.
1 to 10 MΩ	The winding has considerably deteriorated. Special care is required. Be sure to perform a periodic inspection.
Lower than 1 MΩ	Unacceptable.


**Table 1: Insulation resistance ranges according to IEEE 43-2000**

### Applications and Use Case

Insulation measurement is important for end-equipment such as transformers, solar inverters and industrial motor drives (variable speed AC/DC drives and servo drives); see Figures 3 and 4.

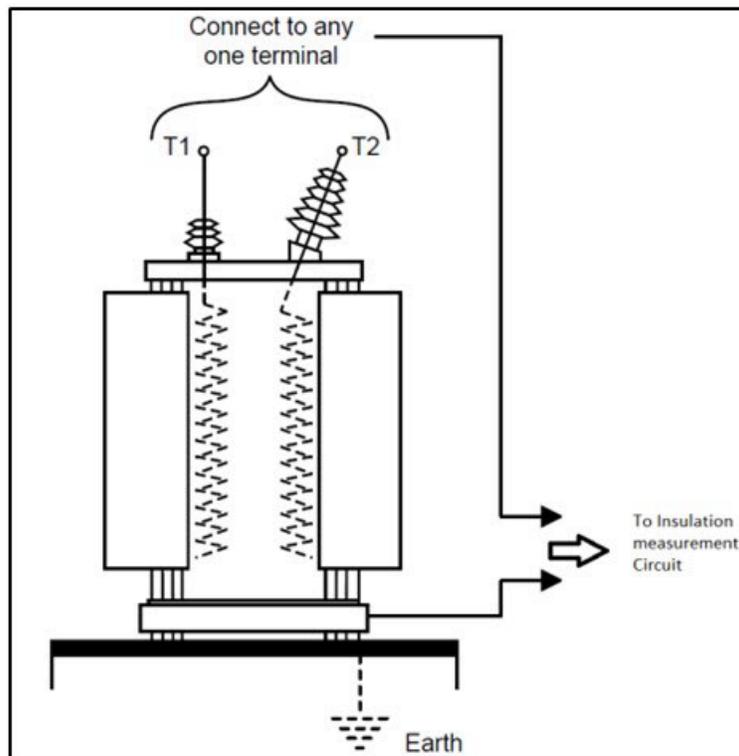


**Figure 3: Measuring the insulation resistance of a high-voltage transformer**

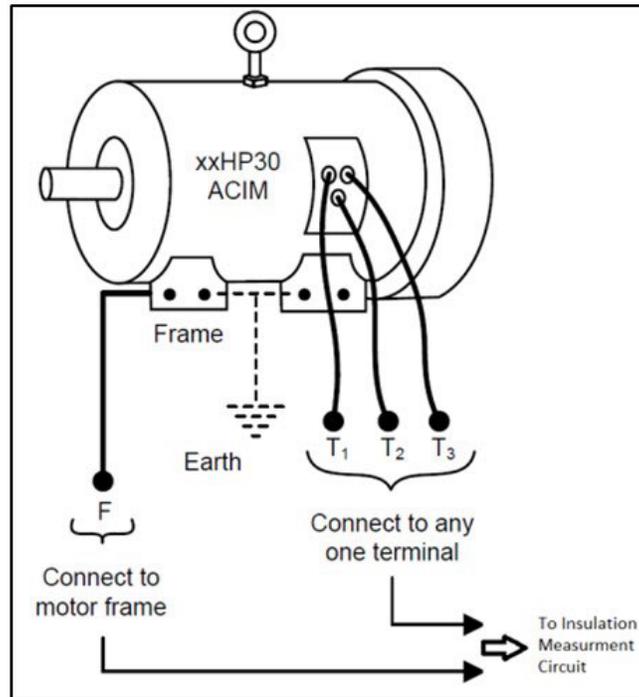


**Figure 4: Measuring the insulation resistance of a motor**

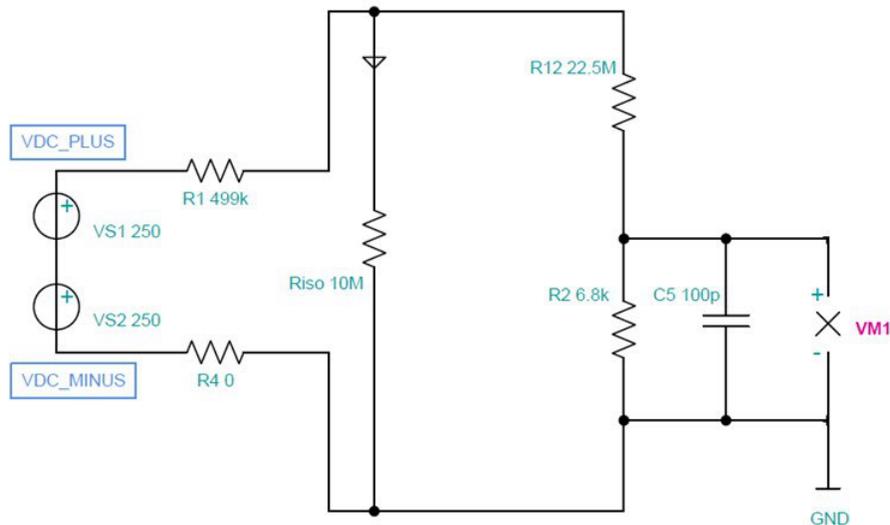Using a resistor divider is a simple way to measure the insulation resistance. Figure 5 shows a TINA-TI™ simulated circuit for this approach, where two series resistors (R12 and R2) are connected in parallel with the insulation resistance (Riso). The total current flowing through the parallel combination is limited by the value of R1, R4 and the DC input (typically 500V according to IEEE 43-2000). The voltage across R2 (which is result of current flow) is measured (VM1), as explained in Fig. 6.




**Figure 5: TINA-TI software simulation of the resistor-divider approach**

Figure 6 is the measurement graph from the TINA-TI simulation. Due to the ratio of resistors, the voltage across R2 does not vary linearly with the insulation resistance (Riso). The measured value of voltage VM1 is almost saturated, with an insulation resistance value greater than 15MΩ.

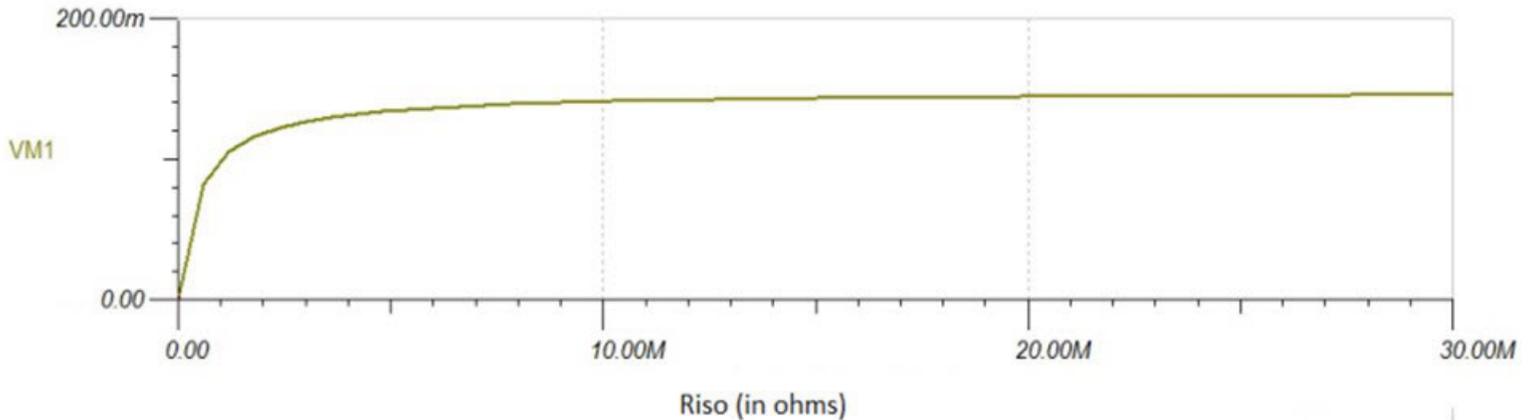

**Figure 6: Graph showing the saturation phenomenon in the resistor-divider approach**

Figure 7 shows the accuracy graph for the resistor-divider approach. The percentage accuracy is < 1% for a range of 0Ω to 22.49MΩ.

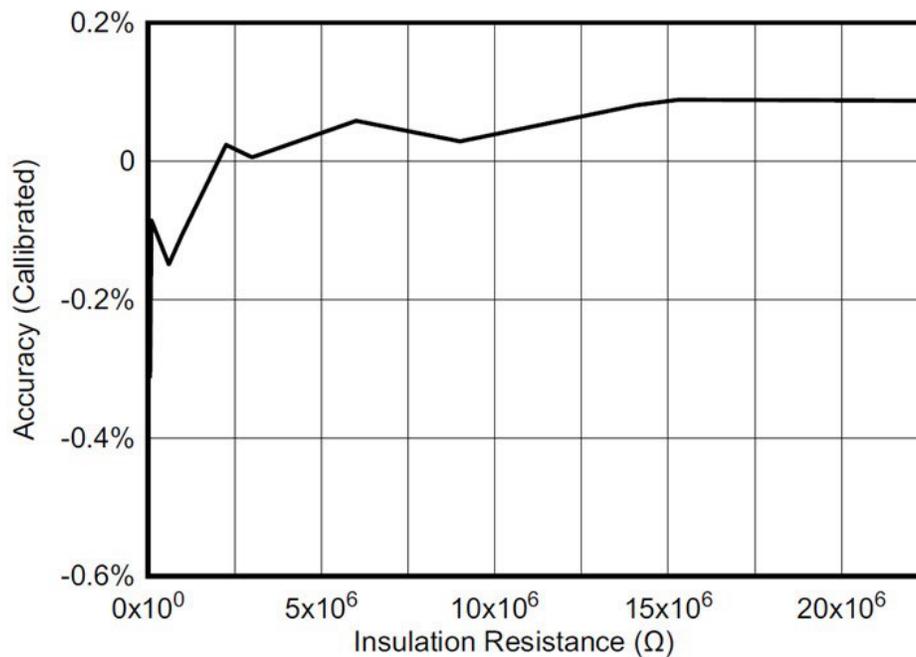

**Figure 7: Accuracy graph for resistor-divider approach**

Table 2 lists the experimental results of this approach. As you can see, the measured output is almost 3mV to 4mV different from the previous value. This difference in value means that a high-resolution analog-to-digital converter (ADC) is required when using the resistor-divider approach, which adds cost to the system.

INSULATION RESISTOR (IN $\Omega$ )	MEASURED OUTPUT VOLTAGE (IN V)
10000	0.0253
100000	0.20254
600000	0.65263
990000	0.79271
2250000	0.97345
3000000	1.0186
6000000	1.09569
9000000	1.1235
14100000	1.14537
15300000	1.14847
22490000	1.1599

**Table 2: Experimental results for the resistor-divider approach**

In my next post, I will look into another method that can offer good accuracy in the entire 0M $\Omega$ -to-100M $\Omega$  range of insulation resistance.

**Additional Resources**

- View the technical documents for the TI Design reference design: [Leakage Current Measurement for Determining Insulation Resistance](#).
- View the [IEEE standard](#).
- Get acquainted with [TINA-TI™ Analog simulation program](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated